

VerilogA Model for 8-bit Asynchronous SAR ADC


MUHAMMAD ALDACHER

3/8/2020

Asynchronous SAR ADC



Asynchronous SAR ADC

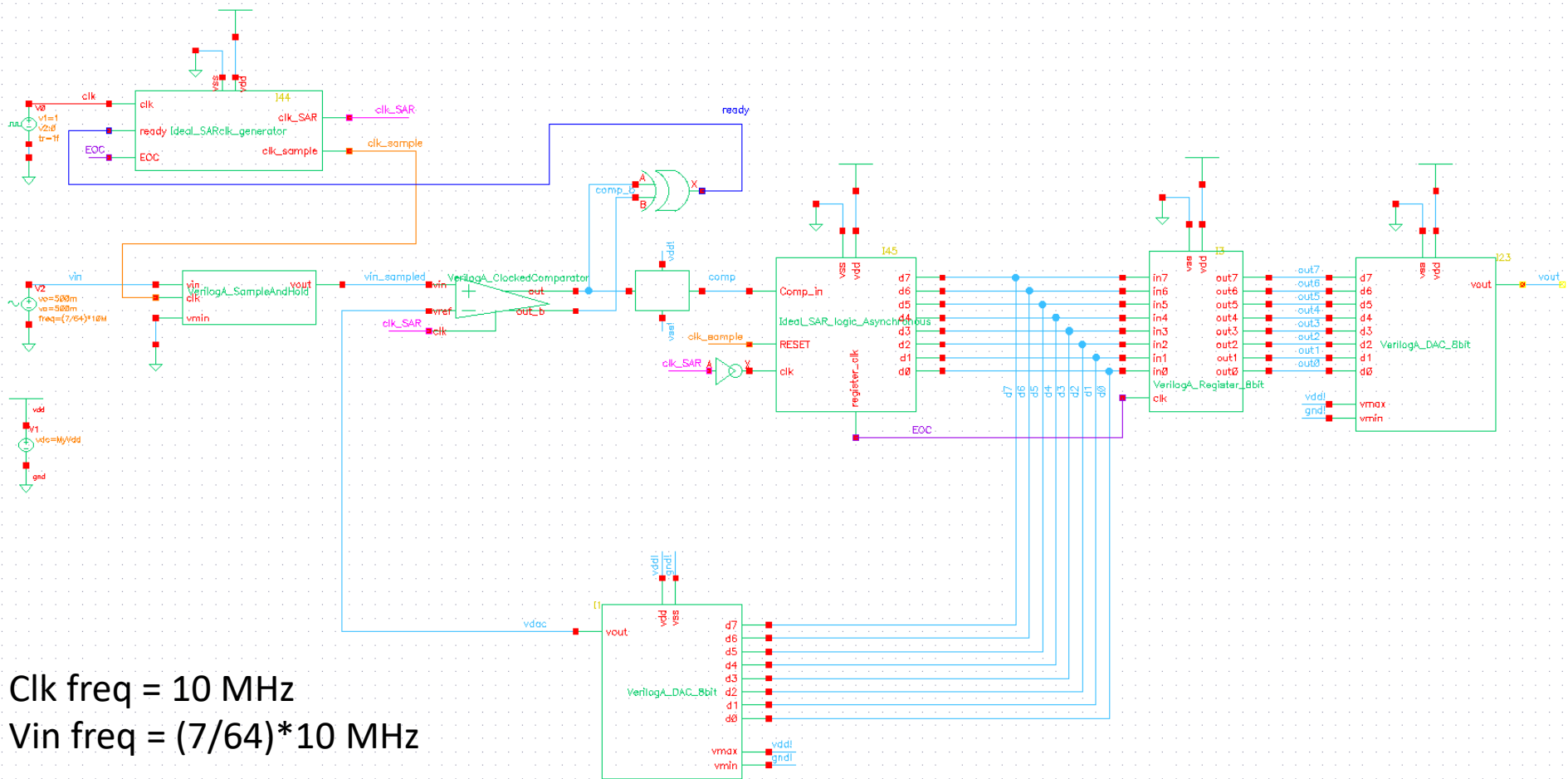


Clk freq = 10 MHz


Vin freq = $(7/64) \times 10\text{ MHz}$

Output = 10 Msamples/sec

Clock-Signals Generator

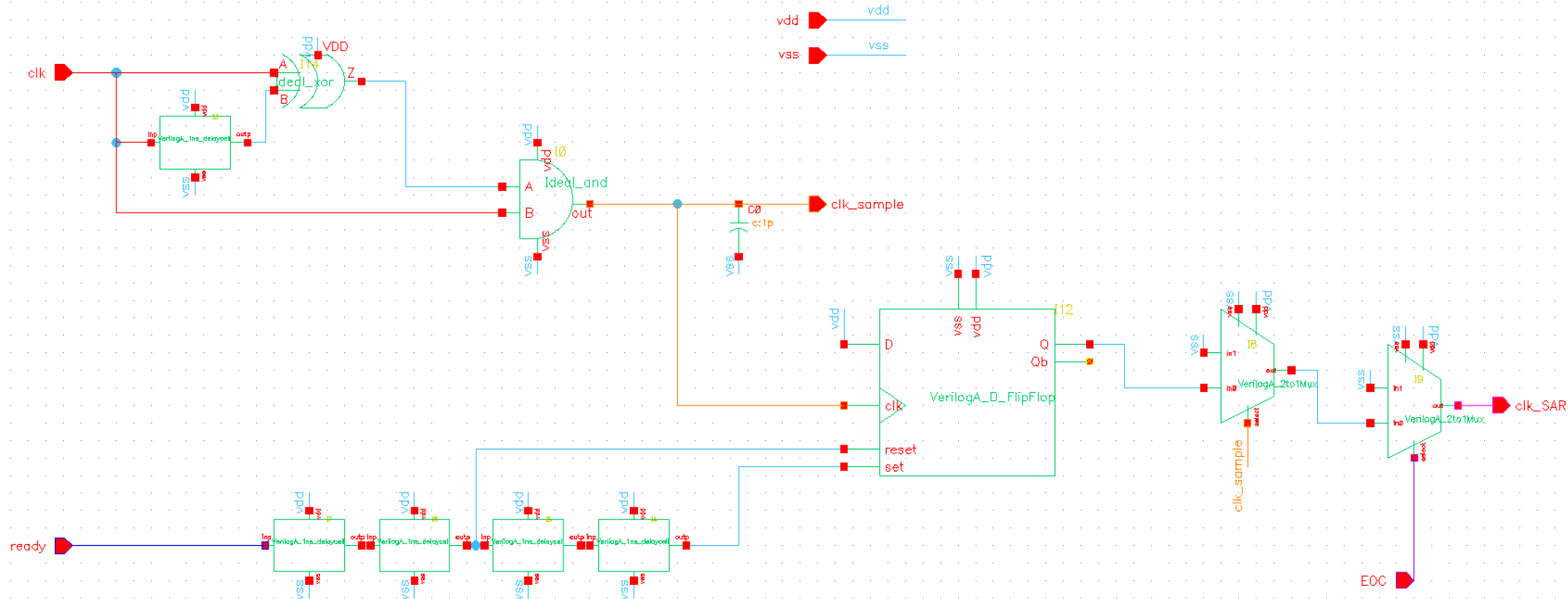


Asynchronous SAR Logic Block

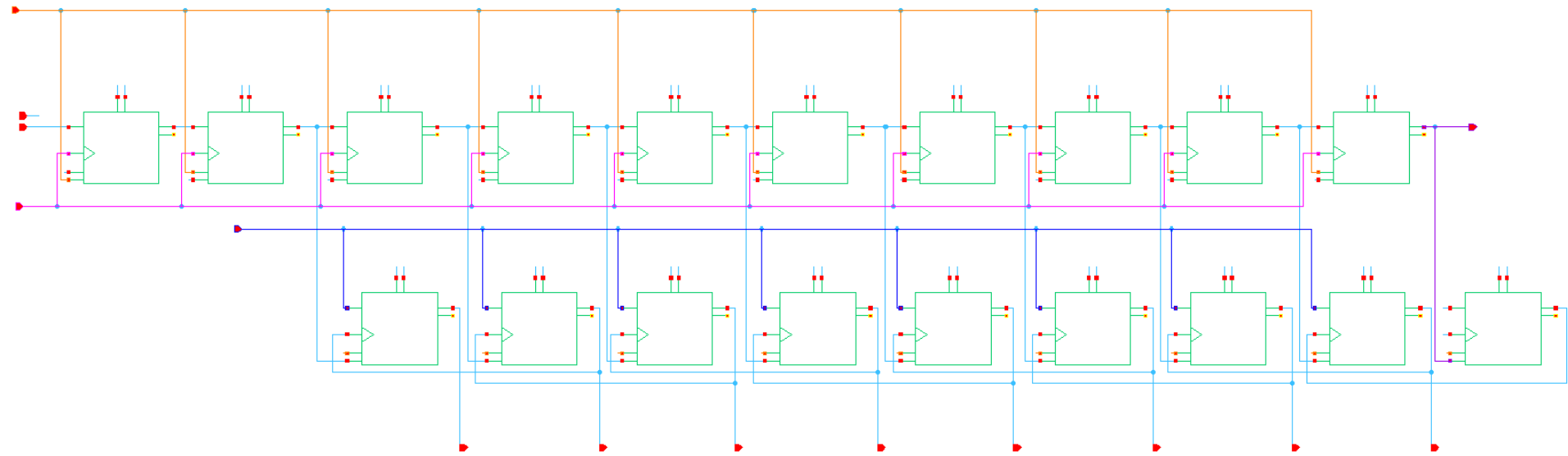

Waveforms

Transient Response


Thu Oct 29 22:30:14 2020

 

Waveforms

Transient Response


Thu Oct 29 22:30:14 2020

 

Waveforms (1 sample cycle)

Transient Response

Thu Oct 29 22:30:14 2020

 

VerilogA Codes

1) Sample-And-Hold

```
// VerilogA for SampleAndHold
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_SampleAndHold(clk,vin,vmin,vout);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;           //vdd is 1v
```

```
input clk,vin,vmin;
```

```
output vout;
```

```
electrical vout,vin,vmin,clk;
```

```
real v;
```

```
analog begin
```

```
    // Sampling Phase (+1 is for rising edge, -1 is for falling edge)
```

```
    @(cross(V(clk) - clk_threshold, +1))
```

```
        v = V(vin);
```

```
    V(vout) <+ transition(v,delay,ttime);
```

```
end
```

```
endmodule
```

2) Clocked Comparator (differential output)

```
// VerilogA for ClockedComparator
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_ClockedComparator(out,out_b,vref,vin,clk);
```

```
parameter real clk_th=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
input vin,vref,clk;
```

```
output out,out_b;
```

```
electrical out,out_b,vref,vin,clk;
```

```
real d_result, d_result_b;
```

```
analog begin
```

```
    @(cross(V(clk) - clk_th, +1)) begin
```

```
        if(V(vin) > V(vref)) begin
```

```
            d_result = 1;
```

```
            d_result_b = 0;
```

```
        end
```

```
        else begin
```

```
            d_result = 0;
```

```
            d_result_b = 1;
```

```
        end
```

```
    end
```

```
    @(cross(V(clk) - clk_th, -1)) begin
```

```
        d_result = 0;
```

```
        d_result_b = 0;
```

```
    end
```

```
    V(out) <+ transition(d_result,delay,ttime);
```

```
    V(out_b) <+ transition(d_result_b,delay,ttime);
```

```
end
```

```
endmodule
```

3) Output Register (8-bit)

```
// VerilogA for SAR_VerilogA, VerilogA_Register_8bit, veriloga

`include "constants.vams"
`include "disciplines.vams"

module
VerilogA_Register_8bit(clk,in0,in1,in2,in3,in4,in5,in6,in7,out0,out1,out
2,out3,out4,out5,out6,out7,vdd,vss);

parameter real vtrans=0.5;
parameter real delay = 0;
parameter real ttime = 1p;
parameter real clk_threshold = 0.5;

inout vdd,vss;
input clk,in0,in1,in2,in3,in4,in5,in6,in7;
output out0,out1,out2,out3,out4,out5,out6,out7;

electrical
clk,in0,in1,in2,in3,in4,in5,in6,in7,out0,out1,out2,out3,out4,out5,out6,o
ut7,vdd,vss;

real d_0,d_1,d_2,d_3,d_4,d_5,d_6,d_7;
```

analog begin

```
@(cross(V(clk) - clk_threshold, +1))
begin
```

```
d_7 = V(in7);
d_6 = V(in6);
d_5 = V(in5);
d_4 = V(in4);
d_3 = V(in3);
d_2 = V(in2);
d_1 = V(in1);
d_0 = V(in0);
```

end

```
V(out7) <+ transition(d_7,delay,ttime);
V(out6) <+ transition(d_6,delay,ttime);
V(out5) <+ transition(d_5,delay,ttime);
V(out4) <+ transition(d_4,delay,ttime);
V(out3) <+ transition(d_3,delay,ttime);
V(out2) <+ transition(d_2,delay,ttime);
V(out1) <+ transition(d_1,delay,ttime);
V(out0) <+ transition(d_0,delay,ttime);
```

```
end
endmodule
```


4) DAC (8-bit)

```
// VerilogA for VerilogA_DAC_8bit
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module
```

```
VerilogA_DAC_8bit(d0,d1,d2,d3,d4,d5,d6,d7,vout,vdd,vss,vmin,vmax);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
inout vdd,vss;
```

```
input d0,d1,d2,d3,d4,d5,d6,d7;
```

```
input vmin, vmax;
```

```
output vout;
```

```
electrical vout,vdd,vss,d0,d1,d2,d3,d4,d5,d6,d7,vmin,vmax;
```

```
real result,d_0,d_1,d_2,d_3,d_4,d_5,d_6,d_7;
```

```
analog begin
```

```
    d_7 = V(d7)*128;
```

```
    d_6 = V(d6)*64;
```

```
    d_5 = V(d5)*32;
```

```
    d_4 = V(d4)*16;
```

```
    d_3 = V(d3)*8;
```

```
    d_2 = V(d2)*4;
```

```
    d_1 = V(d1)*2;
```

```
    d_0 = V(d0)*1;
```

```
    result = ((d_7+d_6+d_5+d_4+d_3+d_2+d_1+d_0) * ((V(vmax)-  
V(vmin))/(256))) + V(vmin) ;
```

```
    V(vout) <+ transition(result,delay,ttime);
```

```
end
```

```
endmodule
```

* D Flipflop (with asynchronous Set & Reset)

```
// VerilogA for SAR_VerilogA, VerilogA_D_FlipFlop, veriloga
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_DFlipFlop(D,clk,Q,Qb,set,reset,vdd,vss);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;
```

```
inout vdd,vss;
```

```
input D,clk,set,reset;
```

```
output Q,Qb;
```

```
electrical D,clk,Q,Qb,set,reset,vdd,vss;
```

```
real d_0,d_0b;
```

```
analog begin
```

```
  @(cross(V(set) - vtrans, +1)) begin
```

```
    d_0 = 1;
```

```
    d_0b = 0; end
```

```
  @(cross(V(reset) - vtrans, +1)) begin
```

```
    d_0 = 0;
```

```
    d_0b = 1; end
```

```
  @(cross(V(clk) - clk_threshold, +1))
```

```
  begin
```

```
    if((V(set) < vtrans) && (V(reset) < vtrans) ) begin
```

```
      if(V(D) > vtrans) begin
```

```
        d_0 = 1; d_0b = 0; end
```

```
      else begin
```

```
        d_0 = 0; d_0b = 1; end
```

```
    end
```

```
  end
```

```
  V(Q) <+ transition(d_0,delay,ttime);
```

```
  V(Qb) <+ transition(d_0b,delay,ttime);
```

```
end
```

```
endmodule
```


* Inverter

```
// VerilogA for SAR_VerilogA_Asynchronous, VerilogA_inv, veriloga
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_inv(A,X);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;
```

```
input A;
```

```
output X;
```

```
electrical A,X;
```

```
real X_out;
```

```
analog begin
```

```
  if(V(A) > vtrans) begin
```

```
    X_out = 0; end
```

```
  else begin
```

```
    X_out = 1; end
```

```
    V(X) <+ transition(X_out,delay,ttime);
```

```
  end
```

```
endmodule
```

* XOR

```
// VerilogA for SAR_VerilogA, VerilogA_XOR, veriloga
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_XOR(A,B,X);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;
```

```
input A,B;
```

```
output X;
```

```
electrical A,B,X;
```

```
real X_out;
```

```
analog begin
```

```
if(V(A) == V(B)) begin
```

```
    X_out = 0; end
```

```
else begin
```

```
    X_out = 1; end
```

```
    V(X) <+ transition(X_out,delay,ttime);
```

```
end
```

```
endmodule
```

* Delay Cell (1ns)

```
// VerilogA for SAR_VerilogA_Asynchronous, VerilogA_1ns_delaycell,  
veriloga
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_1ns_delaycell(inp,outp,vdd,vss);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 1n;
```

```
parameter real ttime = 1f;
```

```
inout vdd,vss;
```

```
input inp;
```

```
output outp;
```

```
electrical inp,outp,vdd,vss;
```

```
real d_out;
```

```
analog begin
```

```
  @(cross(V(inp) - vtrans, +1))
```

```
  begin
```

```
    d_out = 1;
```

```
  end
```

```
  @(cross(V(inp) - vtrans, -1))
```

```
  begin
```

```
    d_out = 0;
```

```
  end
```

```
  V(outp) <+ transition(d_out,delay,ttime);
```

```
end
```

```
endmodule
```

* 2-to-1 Mux

```
// VerilogA for SAR_VerilogA_Asynchronous, VerilogA_2to1Mux, veriloga
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_2to1Mux(in0,in1,select,out,vdd,vss);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;
```

```
inout vdd,vss;
```

```
input in0,in1;
```

```
output out;
```

```
electrical in0,in1,select,out,vdd,vss;
```

```
real result;
```

```
analog begin
```

```
    if(V(select) < vtrans) begin
```

```
        result = V(in0); end
```

```
    else begin
```

```
        result = V(in1); end
```

```
    V(out) <+ transition(result,delay,ttime);
```

```
end
```

```
endmodule
```