


VerilogA Models for 8-bit Synchronous SAR ADC

MUHAMMAD ALDACHER

3/1/2020

Synchronous SAR ADC

Synchronous SAR ADC

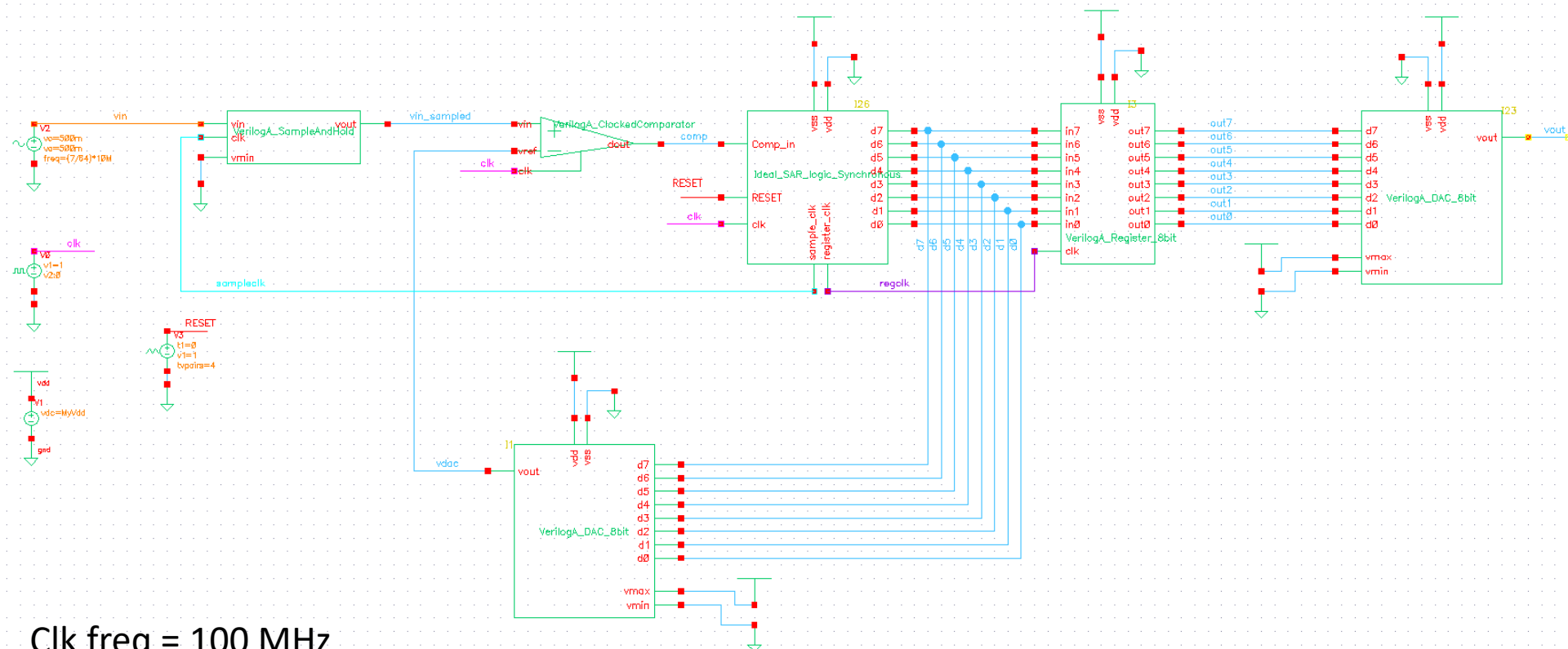


Clk freq = 100 MHz

V_{in} freq = $(7/64) \cdot 10$ MHz

Output = 10 Msamples/sec


Synchronous SAR Logic Block

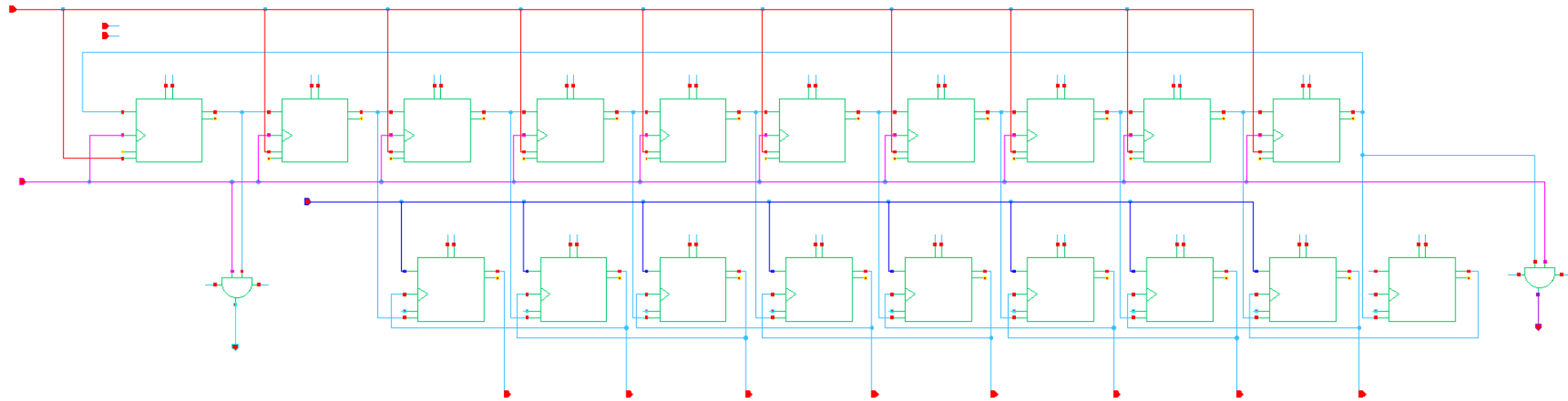

Waveforms

Transient Response


Sun Nov 1 20:28:31 2020

 

Waveforms

Transient Response


Sun Nov 1 20:28:31 2020

 

Waveforms (1 sample)

Transient Response

Sun Nov 1 20:28:31 2020

 

VerilogA Codes

1) Sample-And-Hold

```
// VerilogA for SampleAndHold
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_SampleAndHold(clk,vin,vmin,vout);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;           //vdd is 1v
```

```
input clk,vin,vmin;
```

```
output vout;
```

```
electrical vout,vin,vmin,clk;
```

```
real v;
```

```
analog begin
```

```
    // Sampling Phase (+1 is for rising edge, -1 is for falling edge)
```

```
    @(cross(V(clk) - clk_threshold, +1))
```

```
        v = V(vin);
```

```
    V(vout) <+ transition(v,delay,ttime);
```

```
end
```

```
endmodule
```

2) Clocked Comparator (single output)

```
// VerilogA for ClockedComparator
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_ClockedComparator(dout,vref,vin,clk);
```

```
parameter real clk_th=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
input vin,vref,clk;
```

```
output dout;
```

```
electrical dout,vref,vin,clk;
```

```
real d_result;
```

```
analog begin
```

```
    @(cross(V(clk) - clk_th, -1)) begin
```

```
        if(V(vin) > V(vref)) begin
```

```
            d_result = 1;
```

```
        end
```

```
        else begin
```

```
            d_result = 0;
```

```
        end
```

```
    end
```

```
// We want the comparator to keep its output value when it is in Reset
```

```
    //@(cross(V(clk) - clk_th, +1)) begin
```

```
        //            d_result = 0;
```

```
    //end
```

```
V(dout) <+ transition(d_result,delay,ttime);
```

```
end
```

```
endmodule
```

3) SAR Logic

```
parameter real ttime = 1p;
parameter real clk_threshold = 0.5;
// 8-bits (8-cycles) + 1-cycle for sampling + 1-cycle for Register output = 10-
cycles
```

```
inout vdd,vss;
input in_comp, clk;
output d0,d1,d2,d3,d4,d5,d6,d7;
output sampleclk,regclk;
```

```
electrical in_comp,clk,d0,d1,d2,d3,d4,d5,d6,d7,regclk,sampleclk,vdd,vss;
```

```
real d_0,d_1,d_2,d_3,d_4,d_5,d_6,d_7,sample_en,sar_counter,reg_out;
```

```
analog begin
```

```
    // Initial State
```

```
    @(initial_step) begin
```

```
        sample_en = 1;
```

```
        d_7 = 0;
```

```
        d_6 = 0;
```

```
        d_5 = 0;
```

```
        d_4 = 0;
```

```
        d_3 = 0;
```

```
        d_2 = 0;
```

```
        d_1 = 0;
```

```
        d_0 = 0;
```

```
        sar_counter = 9; //10-bit counter
```

```
    end
```

```
// Operation
```

```
// Comparison
```

```
// At Rising Edge of clk, the bits are updated for comparison.
```

```
// At Falling Edge of clk, the Comparator produces the new bit (Regeneration)
```

```
        @(cross(V(clk) - clk_threshold, +1))
```

```
        begin
```

```
        if(sar_counter == 9) begin
```

```
            sample_en = 1; //1st count is for sampling
```

```
            reg_out = 0;
```

```
                d_7 = 0; d_6 = 0; d_5 = 0; d_4 = 0; d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 0;
```

```
            sar_counter = sar_counter - 1; end
```

```
        else if(sar_counter == 8) begin
```

```
            d_7 = 1; d_6 = 0; d_5 = 0; d_4 = 0; d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 0;
```

```
            sar_counter = sar_counter - 1; end
```

```
        else if(sar_counter == 7) begin
```

```
            d_7 = V(in_comp); d_6 = 1; d_5 = 0; d_4 = 0; d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 0;
```

```
            sar_counter = sar_counter - 1; end
```

```
        else if(sar_counter == 6) begin
```

```
            d_6 = V(in_comp); d_5 = 1; d_4 = 0; d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 0;
```

```
            sar_counter = sar_counter - 1; end
```

```
        else if(sar_counter == 5) begin
```

```
            d_5 = V(in_comp); d_4 = 1; d_3 = 0; d_2 = 0; d_1 = 0; d_0 = 0;
```

```
            sar_counter = sar_counter - 1; end
```

3) SAR Logic “Cont’d”

```

else if(sar_counter == 4) begin
    d_4 = V(in_comp); d_3 = 1; d_2 = 0; d_1 = 0; d_0 = 0;
    sar_counter = sar_counter - 1; end

else if(sar_counter == 3) begin
    d_3 = V(in_comp); d_2 = 1; d_1 = 0; d_0 = 0;
    sar_counter = sar_counter - 1; end

else if(sar_counter == 2) begin
    d_2 = V(in_comp); d_1 = 1; d_0 = 0;
    sar_counter = sar_counter - 1; end

else if(sar_counter == 1) begin
    d_1 = V(in_comp); d_0 = 1;
    sar_counter = sar_counter - 1; end

else if(sar_counter == 0) begin
    d_0 = V(in_comp);
    sar_counter = 9; end
end

// Producing the neg edge of the pulse to sample & to get the output of the
register
@(cross(V(clk) - clk_threshold, -1))
begin
    if(sample_en == 1) begin
        sample_en = 0; end

    if(sar_counter == 0) begin
        reg_out = 1; end
    end
end

V(d7) <+ transition(d_7,delay,ttime);
V(d6) <+ transition(d_6,delay,ttime);
V(d5) <+ transition(d_5,delay,ttime);
V(d4) <+ transition(d_4,delay,ttime);
V(d3) <+ transition(d_3,delay,ttime);
V(d2) <+ transition(d_2,delay,ttime);
V(d1) <+ transition(d_1,delay,ttime);
V(d0) <+ transition(d_0,delay,ttime);
V(regclk) <+ transition(reg_out,delay,ttime);
V(sampleclk) <+ transition(sample_en,delay,ttime);

end

endmodule

```


4) Output Register (8-bit)

```
// VerilogA for SAR_VerilogA, VerilogA_Register_8bit, veriloga
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module
```

```
VerilogA_Register_8bit(clk,in0,in1,in2,in3,in4,in5,in6,in7,out0,out1,out  
2,out3,out4,out5,out6,out7,vdd,vss);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;
```

```
inout vdd,vss;
```

```
input clk,in0,in1,in2,in3,in4,in5,in6,in7;
```

```
output out0,out1,out2,out3,out4,out5,out6,out7;
```

```
electrical
```

```
clk,in0,in1,in2,in3,in4,in5,in6,in7,out0,out1,out2,out3,out4,out5,out6,o  
ut7,vdd,vss;
```

```
real d_0,d_1,d_2,d_3,d_4,d_5,d_6,d_7;
```

```
analog begin
```

```
@(cross(V(clk) - clk_threshold, +1))
```

```
begin
```

```
d_7 = V(in7);
```

```
d_6 = V(in6);
```

```
d_5 = V(in5);
```

```
d_4 = V(in4);
```

```
d_3 = V(in3);
```

```
d_2 = V(in2);
```

```
d_1 = V(in1);
```

```
d_0 = V(in0);
```

```
end
```

```
V(out7) <+ transition(d_7,delay,ttime);
```

```
V(out6) <+ transition(d_6,delay,ttime);
```

```
V(out5) <+ transition(d_5,delay,ttime);
```

```
V(out4) <+ transition(d_4,delay,ttime);
```

```
V(out3) <+ transition(d_3,delay,ttime);
```

```
V(out2) <+ transition(d_2,delay,ttime);
```

```
V(out1) <+ transition(d_1,delay,ttime);
```

```
V(out0) <+ transition(d_0,delay,ttime);
```

```
end
```

```
endmodule
```

5) DAC (8-bit)

```
// VerilogA for VerilogA_DAC_8bit
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module
```

```
VerilogA_DAC_8bit(d0,d1,d2,d3,d4,d5,d6,d7,vout,vdd,vss,vmin,vmax);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
inout vdd,vss;
```

```
input d0,d1,d2,d3,d4,d5,d6,d7;
```

```
input vmin, vmax;
```

```
output vout;
```

```
electrical vout,vdd,vss,d0,d1,d2,d3,d4,d5,d6,d7,vmin,vmax;
```

```
real result,d_0,d_1,d_2,d_3,d_4,d_5,d_6,d_7;
```

```
analog begin
```

```
    d_7 = V(d7)*128;
```

```
    d_6 = V(d6)*64;
```

```
    d_5 = V(d5)*32;
```

```
    d_4 = V(d4)*16;
```

```
    d_3 = V(d3)*8;
```

```
    d_2 = V(d2)*4;
```

```
    d_1 = V(d1)*2;
```

```
    d_0 = V(d0)*1;
```

```
    result = ((d_7+d_6+d_5+d_4+d_3+d_2+d_1+d_0) * ((V(vmax)-  
V(vmin)))/(256))) + V(vmin) ;
```

```
    V(vout) <+ transition(result,delay,ttime);
```

```
end
```

```
endmodule
```


* D Flipflop (with asynchronous Set & Reset)

```
// VerilogA for SAR_VerilogA, VerilogA_D_FlipFlop, veriloga
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VerilogA_DFlipFlop(D,clk,Q,Qb,set,reset,vdd,vss);
```

```
parameter real vtrans=0.5;
```

```
parameter real delay = 0;
```

```
parameter real ttime = 1p;
```

```
parameter real clk_threshold = 0.5;
```

```
inout vdd,vss;
```

```
input D,clk,set,reset;
```

```
output Q,Qb;
```

```
electrical D,clk,Q,Qb,set,reset,vdd,vss;
```

```
real d_0,d_0b;
```

```
analog begin
```

```
  @(cross(V(set) - vtrans, +1)) begin
```

```
    d_0 = 1;
```

```
    d_0b = 0; end
```

```
  @(cross(V(reset) - vtrans, +1)) begin
```

```
    d_0 = 0;
```

```
    d_0b = 1; end
```

```
  @(cross(V(clk) - clk_threshold, +1))
```

```
  begin
```

```
    if((V(set) < vtrans) && (V(reset) < vtrans) ) begin
```

```
      if(V(D) > vtrans) begin
```

```
        d_0 = 1; d_0b = 0; end
```

```
      else begin
```

```
        d_0 = 0; d_0b = 1; end
```

```
    end
```

```
  end
```

```
  V(Q) <+ transition(d_0,delay,ttime);
```

```
  V(Qb) <+ transition(d_0b,delay,ttime);
```

```
end
```

```
endmodule
```